Smart Home Surveillance System v2 - Circuit Wiring

ESP32 DevKit pin map used by smart_home.ino and diagram.json

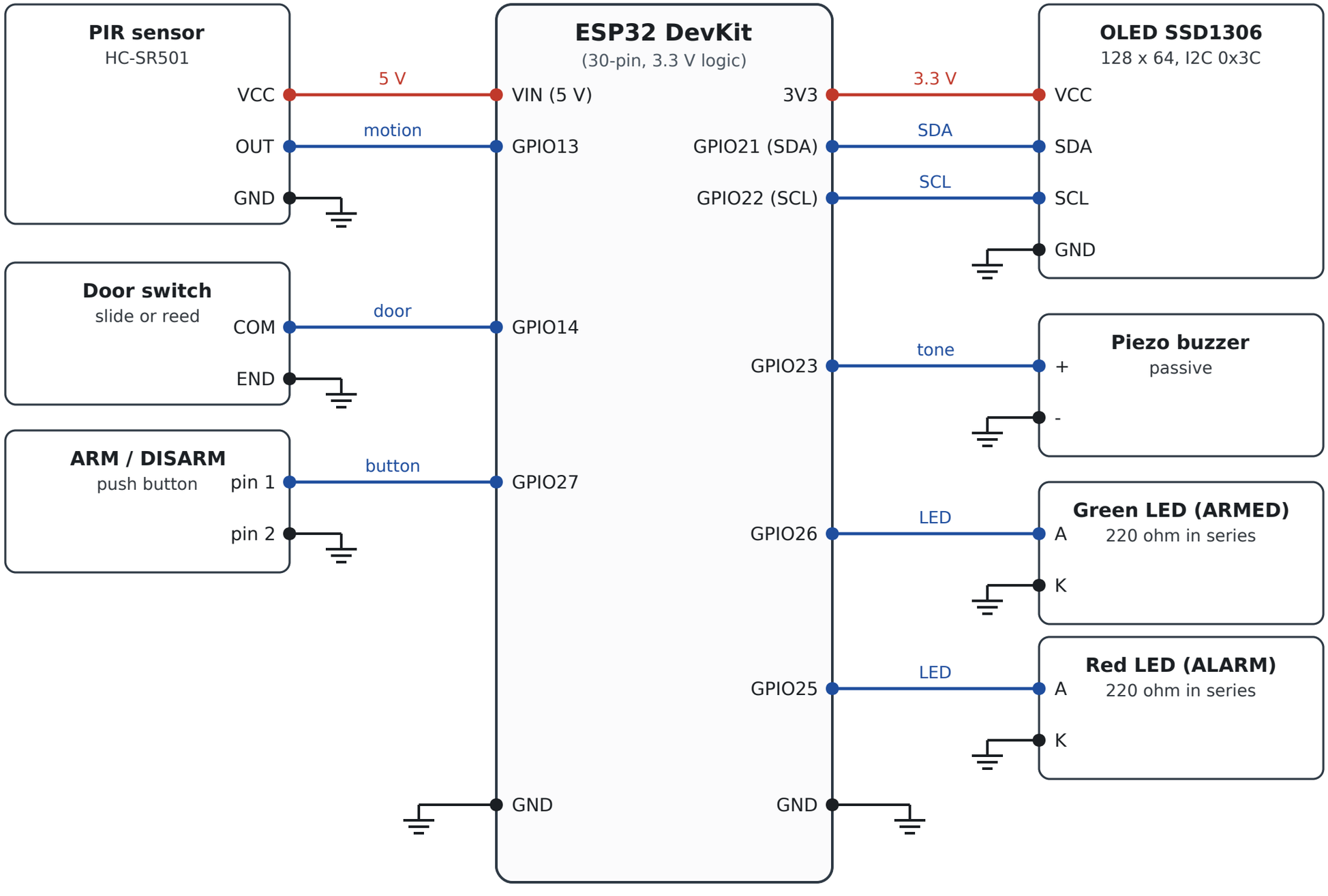

Door switch and button use INPUT_PULLUP: closed / pressed pulls the pin LOW.
The PIR needs 5 V (VIN); its OUT pin is 3.3 V logic, so it is safe for the ESP32.
Use a 220 ohm resistor in series with each LED. None of the pins used here is an ESP32 boot-strapping pin (GPIO0, 2, 5, 12 and 15 are avoided on purpose).